

## **Digital Electronics Class Test :01**

**Answer all the questions**

**5 X 5 = 25**

- Q1. Design a 4-bit Binary to Gray code converter circuit using a suitable PROM.
- Q2. Design a 4-bit Gray to Binary converter circuit using a 3-bit wide AND-OR based PAL.
- Q3. Design a full adder circuit using a suitable PLA.
- Q4. Write the differences between PROM, PAL and PLA.
- Q5. Discuss the advantages of PLDs with Discrete ICs and ASIC.